
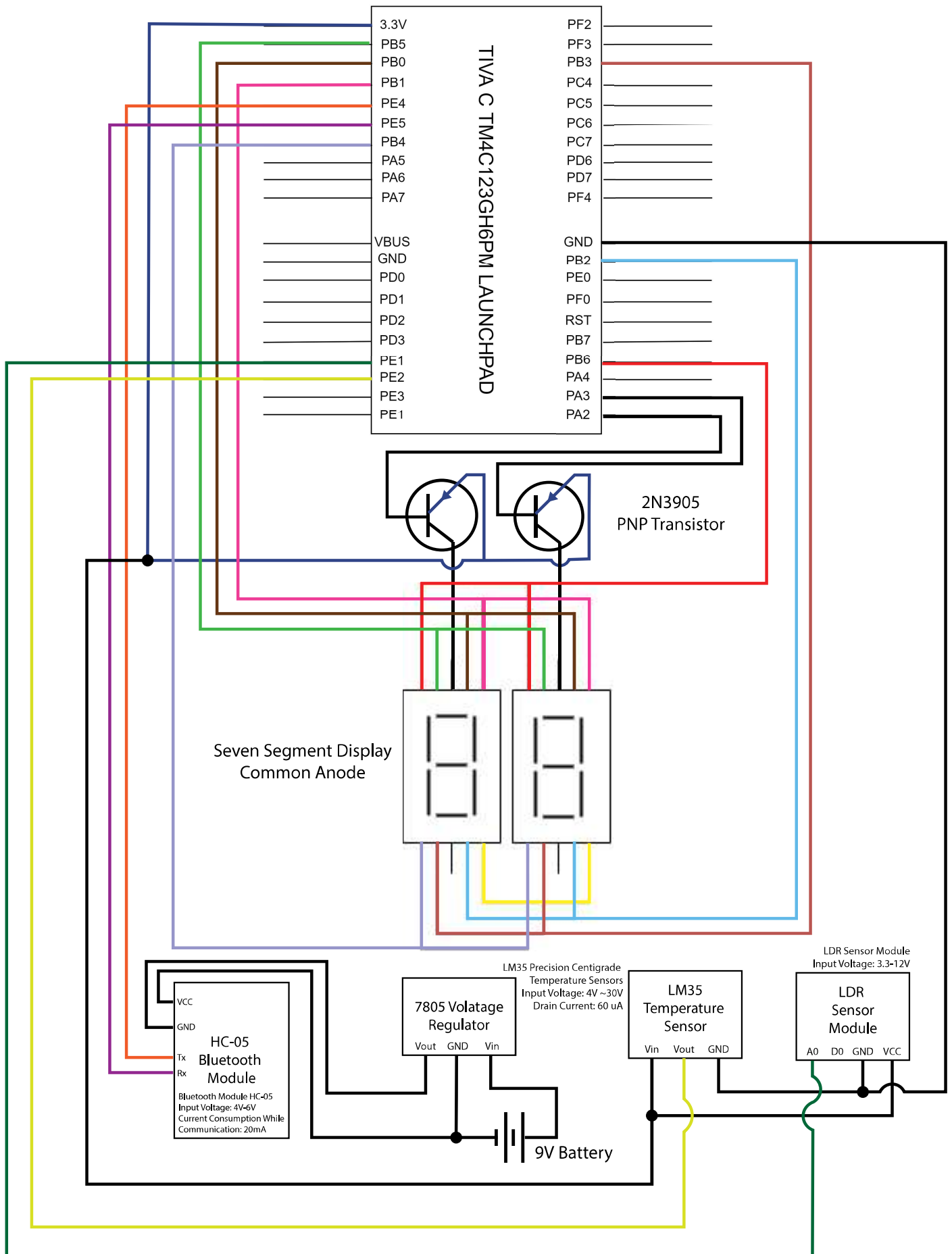


Circuit Diagram

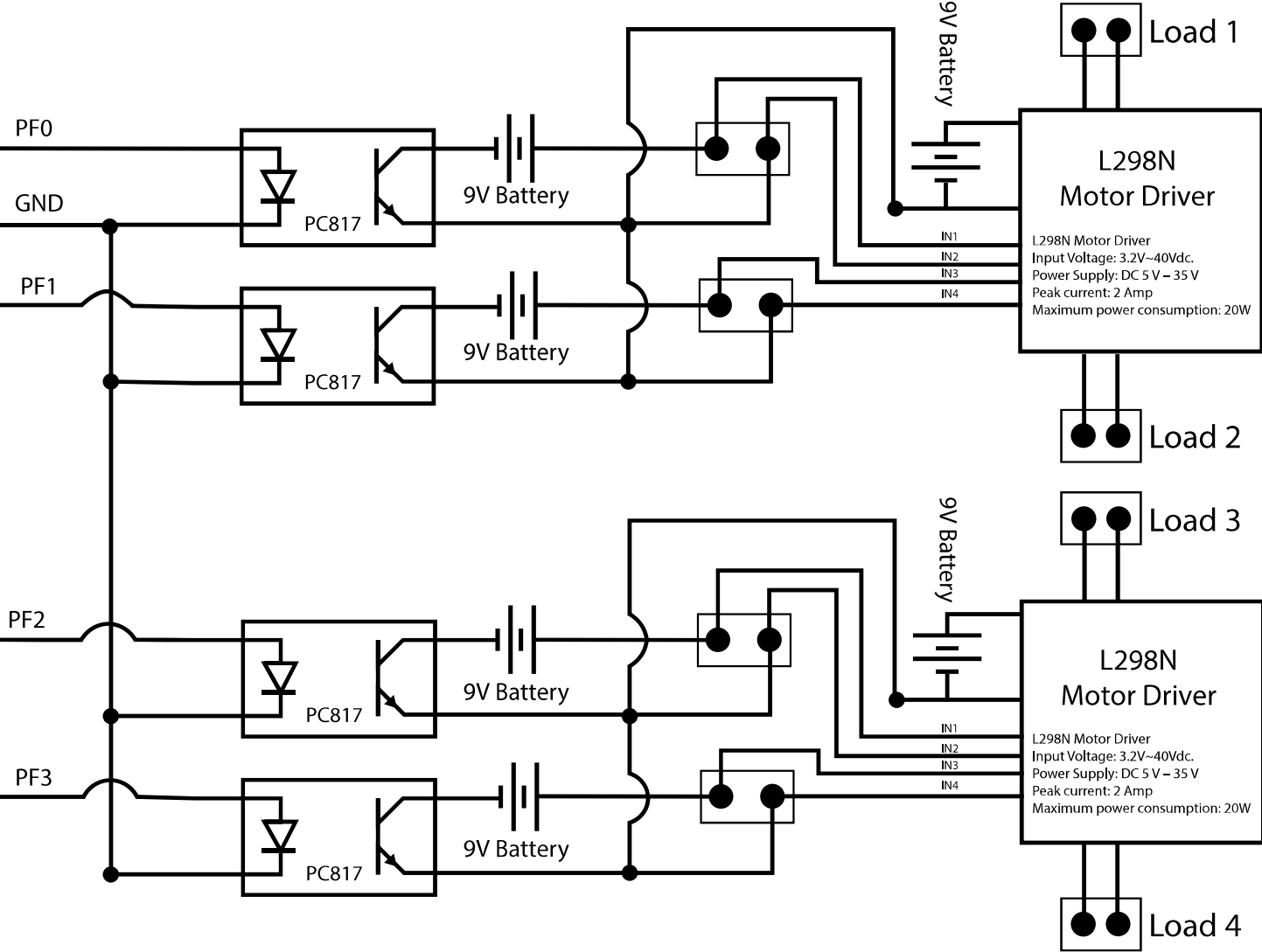

*Different colors are used to differentiate different wires and avoid confusion and messy connections

Connection with L98N Motor Driver



PCB Design

